



India's **Most Comprehensive** & the **Most Relevant**
Test Series designed according to the latest pattern of exams!



JEE MAIN



JEE ADV.



BITSAT



WBJEE



MHT CET

and many more...

[Click here to join Test Series for 2022](#)

It's time for you to crack upcoming IIT JEE Main & Advanced and other competitive exams with India's Most Trusted Online Test Series. **Many questions at JEE Main 2021 were same/similar to the ones asked in our test series.** That's the power of our test series!

Trusted by **thousands of students**
& **their parents** across the nation

Our result in JEE Main 2021

150+

Got **99+ percentile** (overall)

301

Got **99+ percentile** in one or more subjects

85%

Improved their score by **25 percentile**

89%

Felt **overall confident** after the test series

[Click here to join Test Series for 2022](#)



FREE Question Bank & Previous Year Questions for



JEE MAIN



JEE ADV.



BITSAT



WBJEE




MHT CET

and many more...



Click on this button

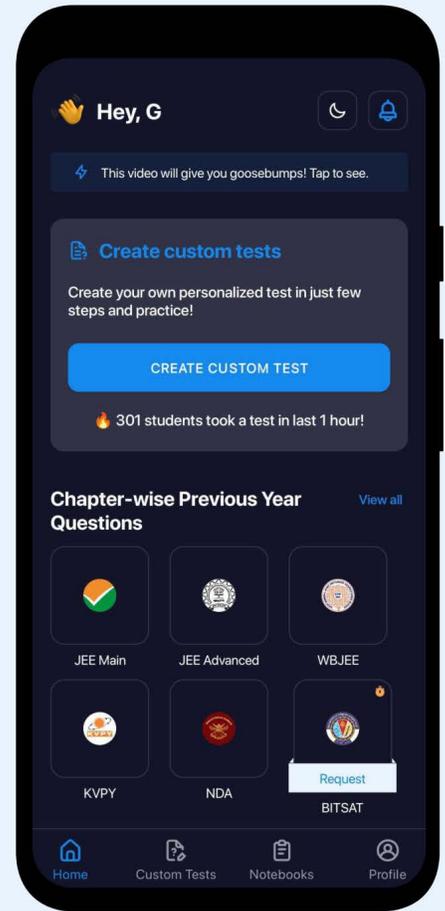

😎 Why download MARKS?

- 📖 Chapter-wise PYQ of JEE Main, JEE Advanced, NEET, AIIMS, BITSAT, WBJEE, MHT CET etc.
- 📖 Chapter-wise NTA Abhyas questions
- 🎯 Daily practice challenge and goal completion
- 📌 Bookmark important questions and add them to your notebooks
- 👉 Create unlimited Custom Tests

And all this for **FREE**. Yes, **FREE**! So what are you waiting for, download MARKS now.

4.8

Rating on Google Play

30,000+

Students using daily

1,00,000+

Questions available




Click on this button

LOGIC GATES

OR Gate :

Boolean expression $Y = A + B$

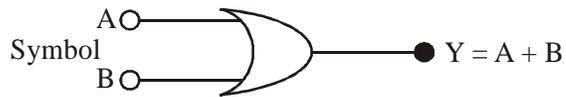

Truth table

A	B	Y
0	0	0
1	0	1
0	1	1
1	1	1

AND gate

Boolean expression $Y = A \cdot B$




Truth table

A	B	Y
0	0	0
1	0	0
0	1	0
1	1	1

NOT gate

Boolean expression $Y = \bar{A}$

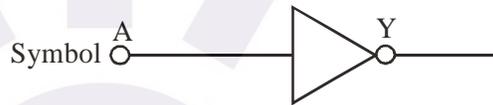

Truth table

A	Y
0	1
1	0

NAND gate

Boolean expression $\overline{A \cdot B}$




Truth table

A	B	Y
0	0	1
1	0	1
0	1	1
1	1	0

NOR gate

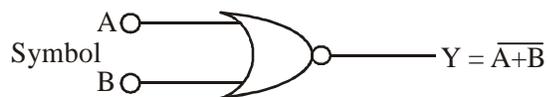Boolean expression $Y = \overline{A + B}$



Truth table

A	B	Y
0	0	1
1	0	0
0	1	0
1	1	0

XOR gate or Ex-OR gate

Boolean expression $Y = A\bar{B} + \bar{A}B$




Truth table

A	B	Y
0	0	0
1	0	1
0	1	1
1	1	0

NAND and NOR work as basic building blocks

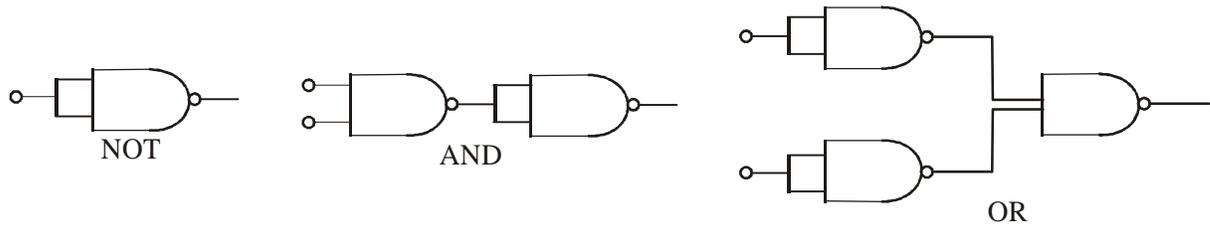Any logic gate can be realised by using only NAND gates or only NOR gates. Therefore these two gates are called the building blocks NAND / NOR are also universal gate.



Quizrr